

--	--	--	--	--	--	--	--

B.Tech. Degree III Semester Regular/Supplementary Examination February 2022

CS 19-202-0302 LOGIC DESIGN (2019 Scheme)

Time: 3 Hours

Maximum Marks: 60

PART A (Answer *ALL* questions)

(8 × 3 = 24)

- I. (a) Given the two binary numbers $X = 1010100$ and $Y = 1000011$, perform the subtraction:

- (i) $X - Y$ and
(ii) $Y - X$ by using 2's complements.

- (b) Show that the dual of the exclusive-OR is equal to its complement.
(c) Design a 4 × 16 decoder using two 3 × 8 decoders.
(d) Design a 4 bit shift register with serial input and serial output.
(e) A 12-bit Hamming code word containing 8 bits of data and 4 parity bits is read from memory. What was the original 8-bit data word that was written into memory for the following codes.

- (i) 000011101010
(ii) 101110000110
(iii) 101111110100

- (f) What are the basic differences between PROM, PLA and PAL?
(g) Define the following and provide the values of each for ECL and CMOS logic.

- (i) Fan out
(ii) Propagation delay
(iii) Noise margin.

- (h) Tabulate the truth table for an 8 × 4 ROM that implements the Boolean functions.

$$\begin{aligned} A(x, y, z) &= \Sigma(0, 3, 4, 6) \\ B(x, y, z) &= \Sigma(0, 1, 4, 7) \\ C(x, y, z) &= \Sigma(1, 5) \\ D(x, y, z) &= \Sigma(0, 1, 3, 5, 7) \end{aligned}$$

PART B

(4 × 12 = 48)


- II. (a) Simplify the following expression using the K-Map method by finding essential prime implicants. (6)

$$\begin{aligned} F(A, B, C, D) &= \Sigma(5, 6, 7, 12, 14, 15) \\ d(A, B, C, D) &= \Sigma(3, 9, 11) \end{aligned}$$

- (b) Implement the Boolean function $F = xy + x'y' + y'z$ (6)

- (i) With OR and inverter gates only
(ii) With AND and inverter gates only
(iii) With NOR and inverter gates only.

OR

 

BTS-III(R/S)-02-22-0003

III. (a) Simplify the following Boolean function into (6)

- (i) sum-of-products form
(ii) product-of-sums forms.

$$F(A, B, C, D) = \sum (0, 1, 2, 5, 8, 9, 10)$$

(b) Simplify the following Boolean function using the Quine McCluskey method. (6)

$$F(A, B, C, D) = \sum (2, 3, 4, 5, 6, 7, 9, 11, 12, 13)$$

IV. (a) Implement the following four Boolean expressions with three half adders: (6)

$$\begin{aligned} D &= A \oplus B \oplus C \\ E &= A'BC + AB'C \\ F &= ABC' + (A' + B')C \\ G &= ABC \end{aligned}$$

(b) Implement the following Boolean function with a multiplexer (6)

$$F(A, B, C, D) = \sum (0, 2, 5, 8, 10, 14)$$

OR

V. (a) What is Carry Propagation delay? Design a 4-bit binary parallel adder with look ahead carry generator. (6)

(b) Design a code converter that converts a decimal digit from 8,4,-2,-1 code to BCD. (6)

VI. (a) Design a synchronous counter using T flip-flops which counts the following repeated binary sequence: 0,1,2,4,6. Derive a suitable self-correcting method for invalid states. (6)

(b) Design a BCD ripple counter using JK flip-flops. (6)

OR

VII. (a) Draw the logic diagram of a four-bit binary ripple counter. Show that a BCD ripple counter can be constructed from this counter with asynchronous clear and a NAND gate. (6)

(b) Design a 4 bit ring counter. How does it differ from a Johnson counter? (6)

VIII. (a) Design a PLA circuit to implement the functions (6)

$$F_1 = A'B + AC + A'BC$$

$$F_2 = (AC + AB + BC)'$$

(b) What is meant by address multiplexing? With a neat diagram, illustrate how address multiplexing is done for a 64K DRAM. (6)

OR

IX. (a) Draw circuit of an TTL NAND gate and explain the operation. (7)

(b) Compare the performances of CMOS and TTL logic. (5)
